

NAME : PRATHAPANI SATWIKA

REG.NO. : 20BCD7160

EXPERIMENT NO. -7

Objective : To study the input and output characteristics of semiconductor diodes

Software Used : NI Multisim 14.0

Theory :

A semiconductor diode is a combination of p and n type semiconductors which in forward bias at which the flow of current during the PN Junction begins increasing rapidly is known as **cut-in voltage** . After achieving cutting voltage the increase in current is almost exponential . A diode in reverse bias conducts negligible amount of current in the order of micro amperes .

$$I = I_0 (e^{(V/(\eta V_T))} - 1)$$

Where ,

I = current flowing through the diode

I_0 = reverse saturation current,

q = charge on the electron,

V = voltage applied across the diode,


η = ideality factor (Ge = 1 and Si = 2) .

T is the absolute temperature in Kelvin.


The configuration in which the emitter is connected between the collector and base is known as a common emitter configuration. The input circuit is connected between emitter and base , and the output circuit is taken from the collector and emitter .

Circuit Diagram :


1 . Diode in Forward Bias :

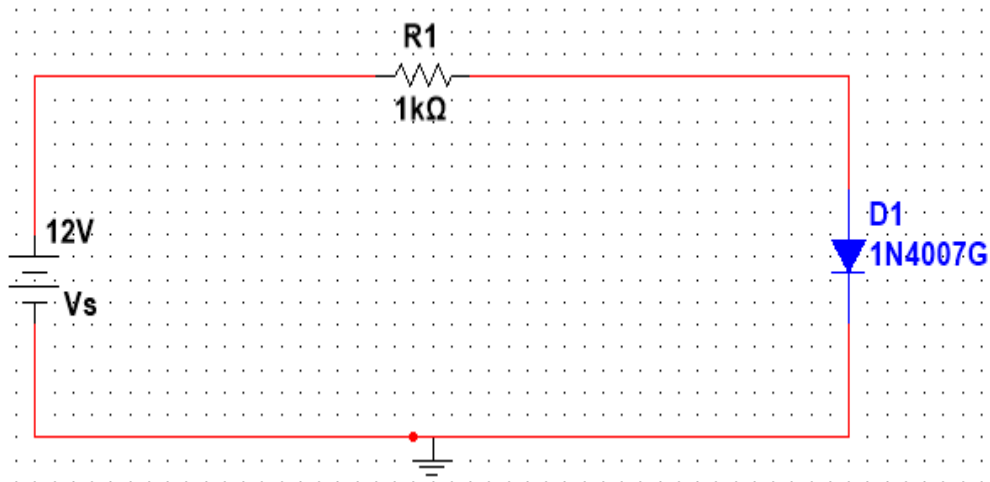

2 . Diode in Reverse Bias :

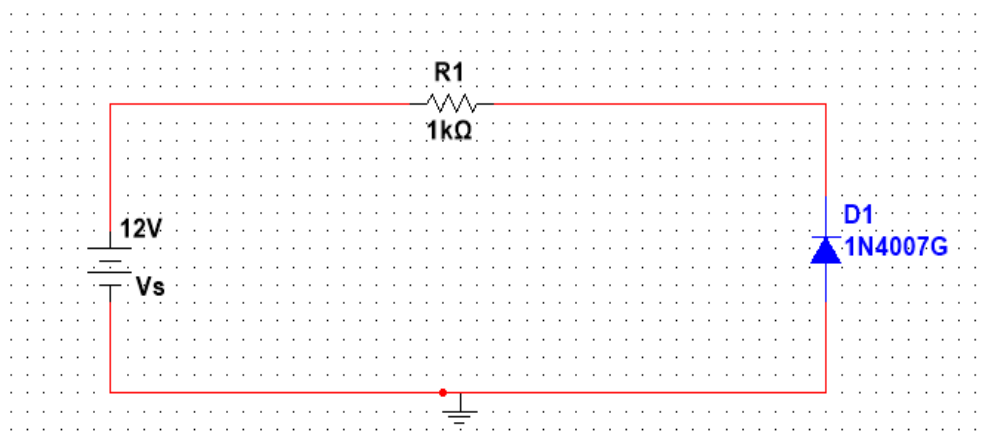

3 . Common Emitter Configuration :

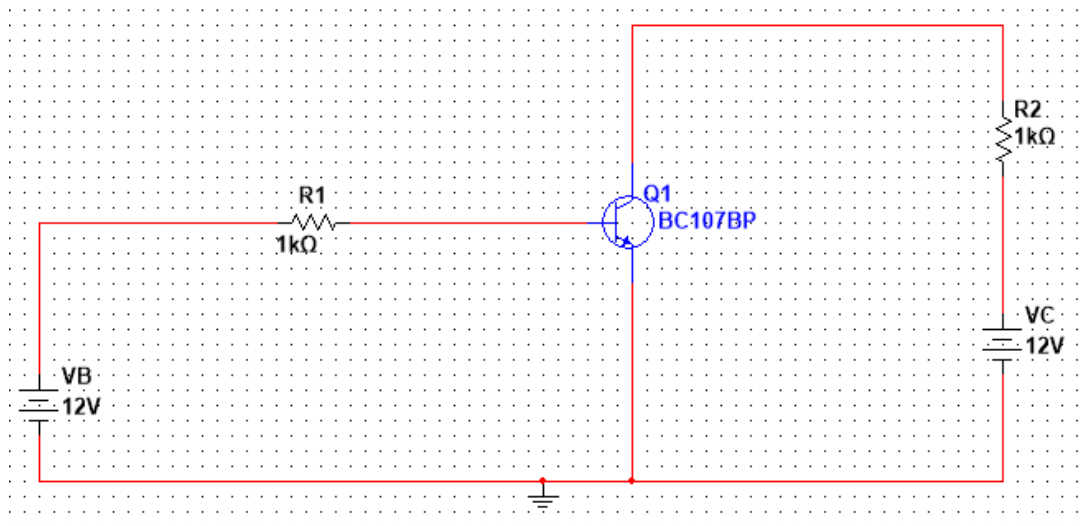


Results & Observations :

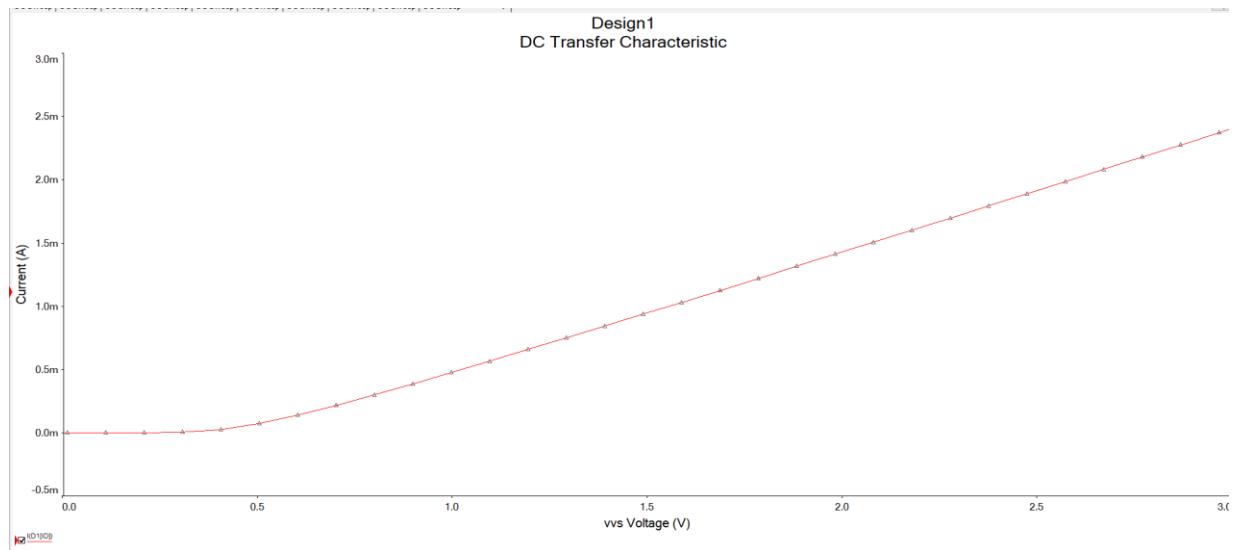1 . Diode is in Forward Bias :


The Cutting Voltage for the diode is 0.3 V .

Therefore the diode is a Germanium Diode .




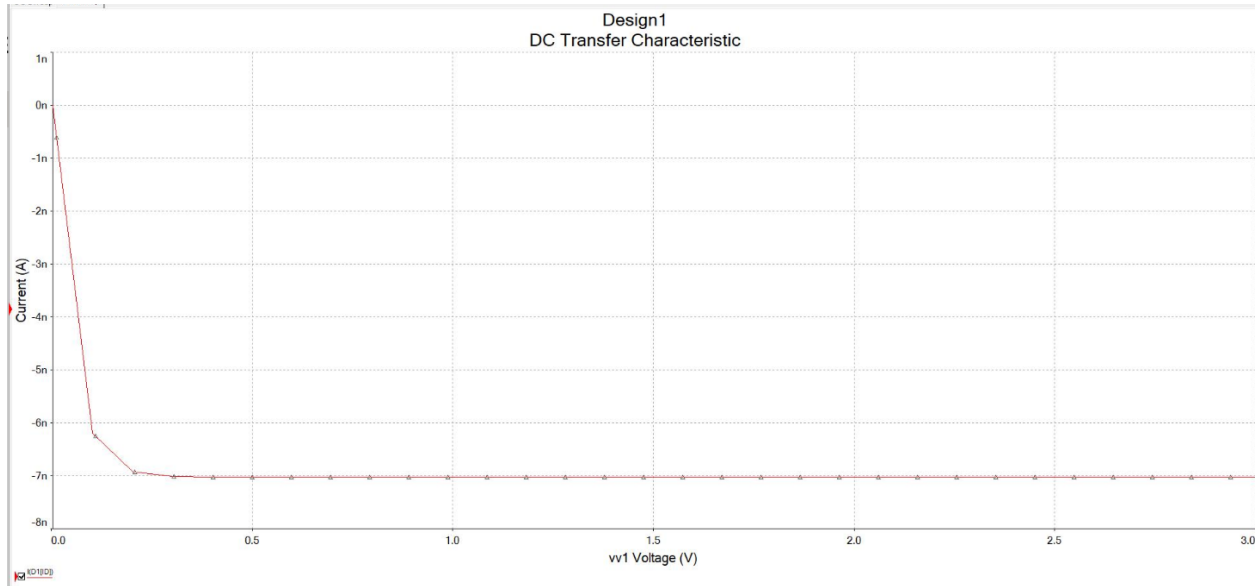2 . Diode is in Reverse Bias :

The leakage current is negligible or zero .




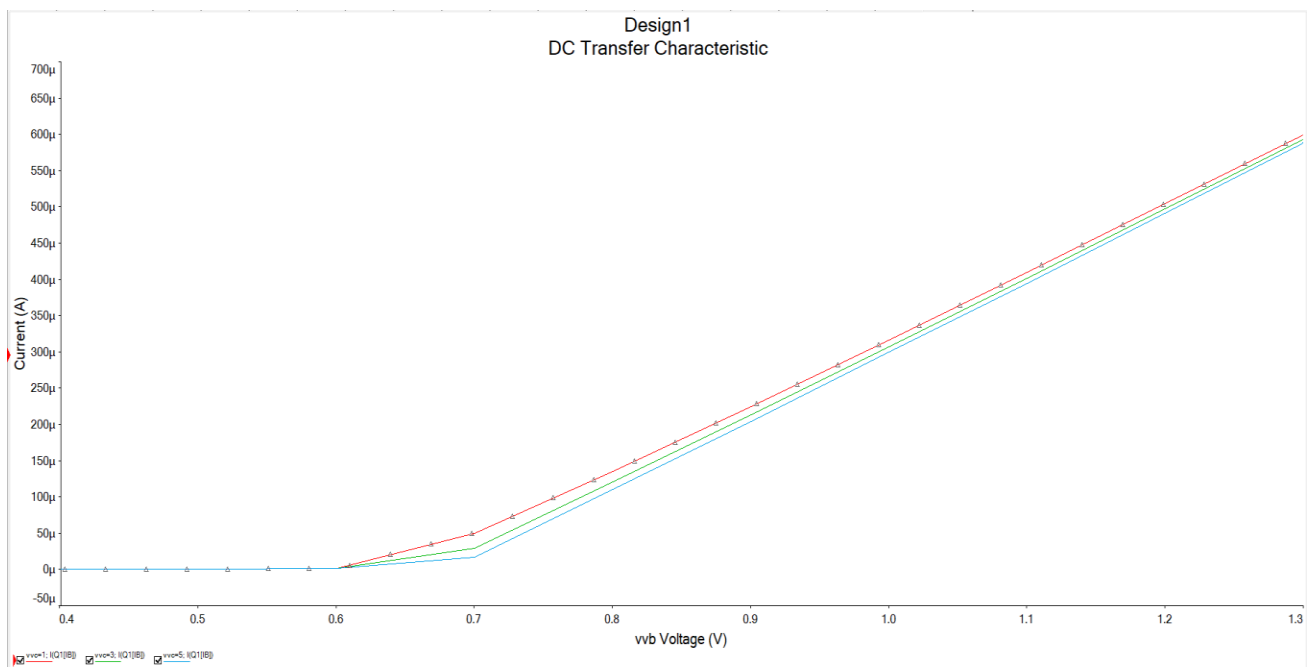3 . Common Emitter Configuration Input Characteristics :



	Voltage (V_C)		
	1V	3V	5V
Cutting Voltage (V_γ)	0.500V	0.506V	0.510V

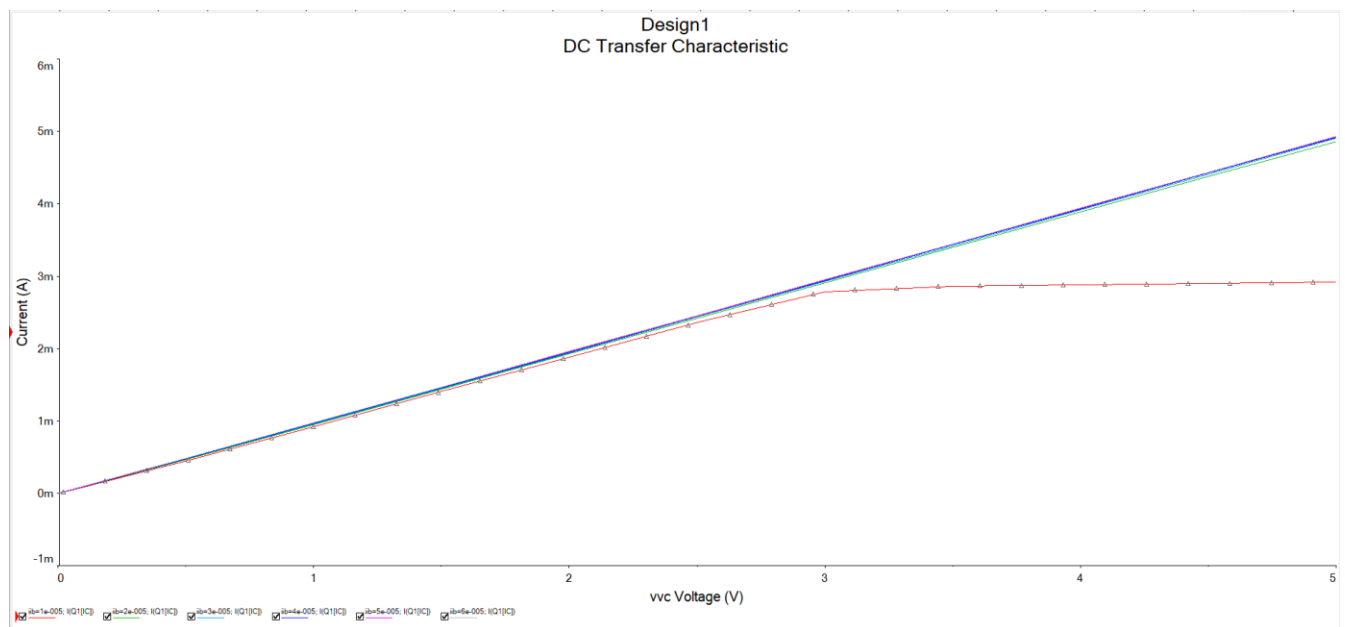4 . Common Emitter Configuration Output Characteristics :



	Base Current (I_B)		
	10 μ A	30 μ A	50 μ A
Collector Current (I_C)	2.77mA	8.74mA	14.46mA

EXPERIMENT NO. – 8

Objective : To design and simulate the half wave rectifier and full wave rectifier.

Software used : NI Multisim

Theory :

A rectifier is a circuit that converts the Alternating Current (AC) input power into a Direct Current (DC) output power.

Half wave rectifiers use one diode, while a full wave rectifier uses multiple diodes.

“ The power diode in a half-wave rectifier circuit passes just one half of each complete sine wave of the AC supply to convert it into a DC supply. Then this type of circuit is called a “ **Half-wave rectifier** ”, because it passes only half of the incoming AC power supply ” .


During each “ positive ” half cycle of the AC sine wave, the diode is forward biased as the anode is positive concerning the cathode resulting in current flowing through the diode. During each “ negative ” half cycle of the AC sinusoidal input waveform, the diode is reverse biased as the anode is negative concerning the cathode. Therefore, NO current flows through the diode or circuit .

“ **Full-wave rectifier** rectifies the negative component of the input voltage to a positive voltage then converts it into DC current utilizing a diode **bridge** configuration ” .


“ **Bridge rectifier** can be defined as a type of full-wave rectifier that uses four or more diodes in a bridge circuit configuration to efficiently convert alternating (AC) current to a direct (DC) current ” .

Circuit Diagram :


1 . Half Wave Rectifier :

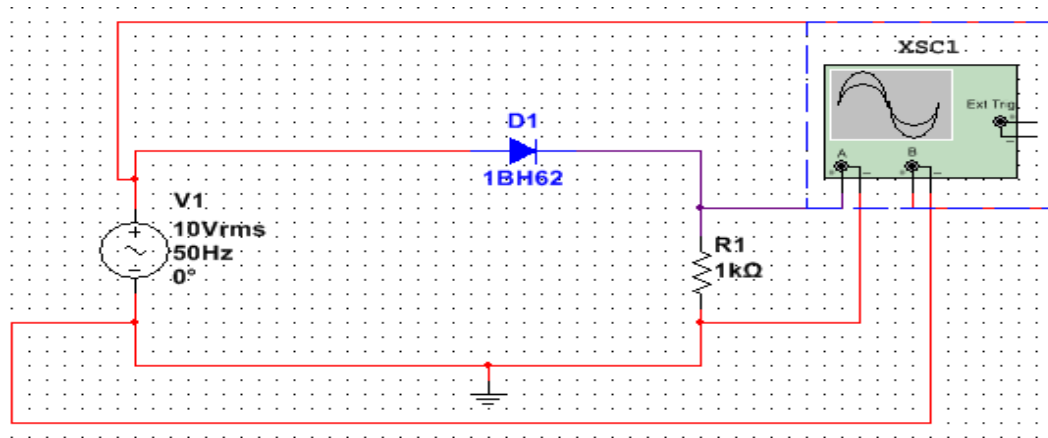


Graph :

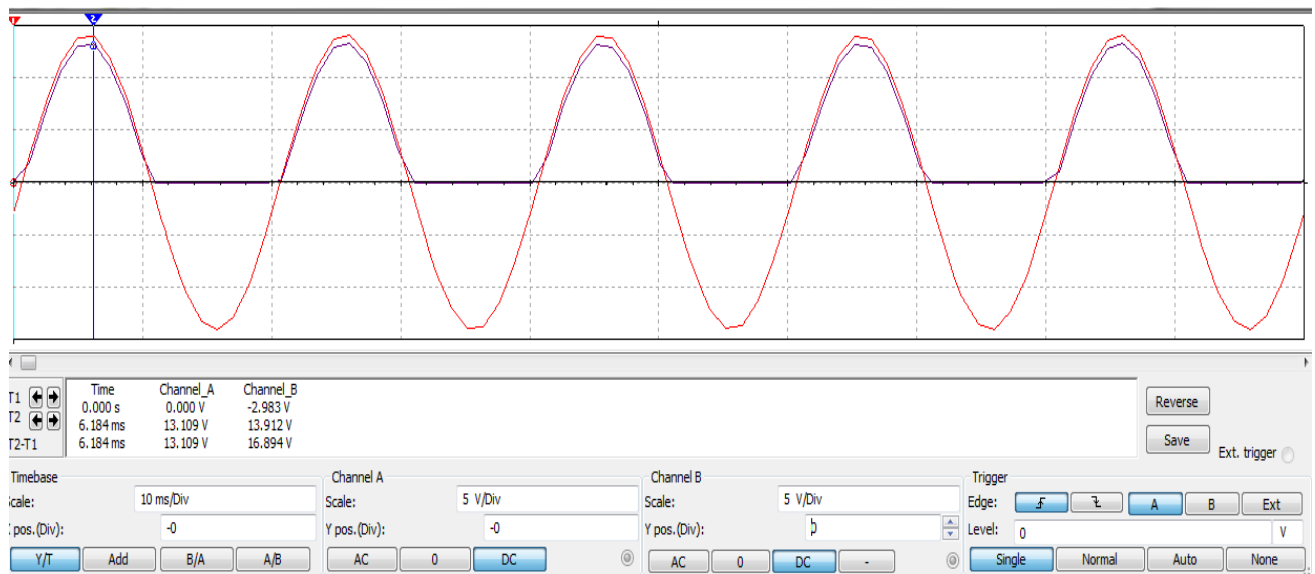

2 . Full Wave Rectifier :

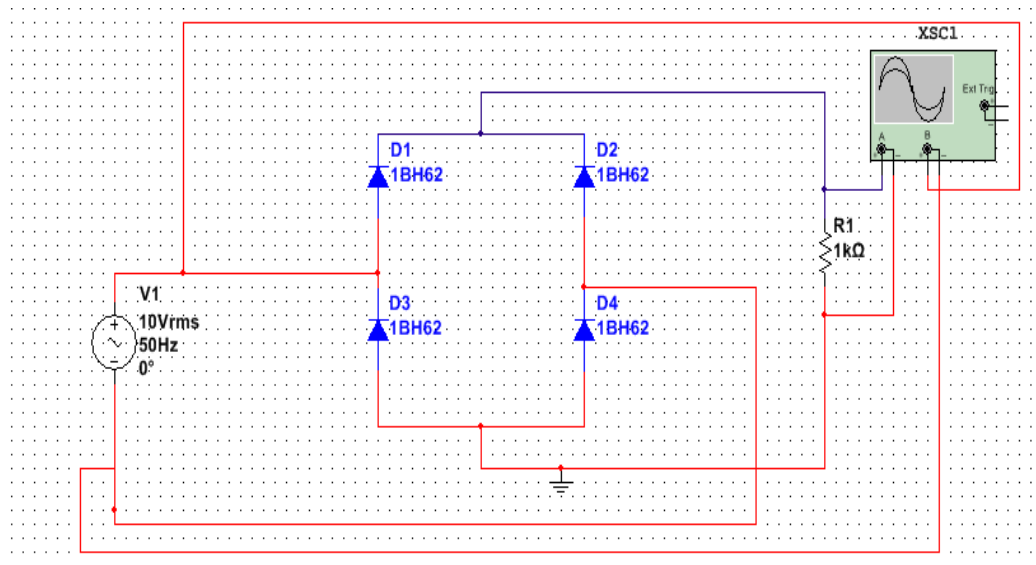

Graph :

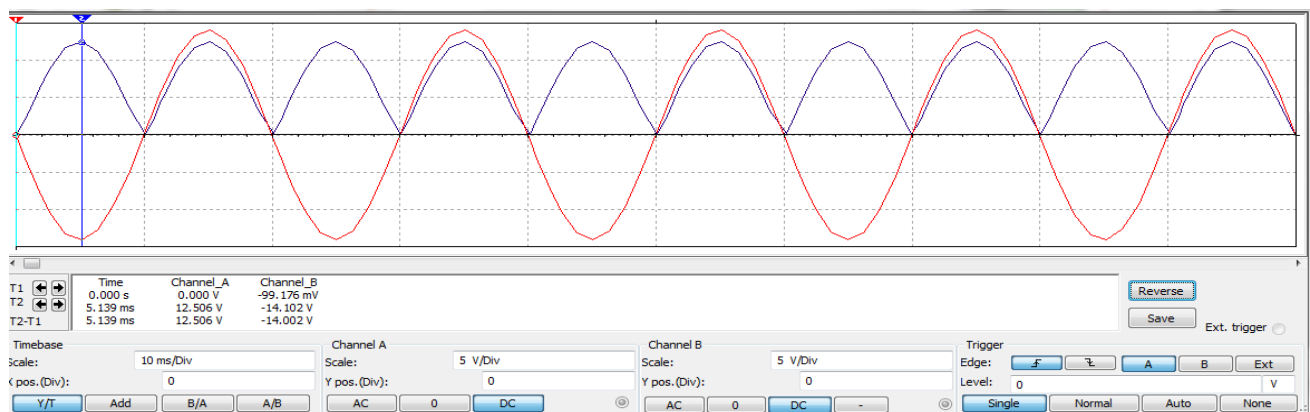

Results & observations :

Half wave Rectifier :

Theoretical values :

$$V_m = 10\sqrt{2} \text{ V}$$

$$V_{rms} = V_m/2 = 10\sqrt{2}/2 = 7.07 \text{ V}$$

$$V_{DC} = V_m/\pi = 14.14/\pi = 4.50 \text{ V}$$

$$\gamma = \sqrt{(V_{rms}/V_{DC})^2 - 1}$$

$$= 1.211$$

Experimental Values :

$$V_m = 13.109 \text{ V}$$

$$V_{rms} = V_m/2 = 13.109/2 = 6.55 \text{ V}$$

$$V_{DC} = V_m/\pi = 13.109/\pi = 4.172 \text{ V}$$

$$\gamma = \sqrt{(V_{rms}/V_{DC})^2 - 1}$$

$$= 1.210$$

Full Wave Rectifier :

Theoretical values :

$$V_m = 10\sqrt{2} = 14.14 \text{ V}$$

$$V_{rms} = V_m/\sqrt{2} = 10 \text{ V}$$

$$V_{DC} = 2V_m/\pi = 9.003 \text{ V}$$

$$\gamma = \sqrt{(V_{rms}/V_{DC})^2 - 1}$$
$$= 0.483$$

Experimental Values :

$$V_m = 12.506 \text{ V}$$

$$V_{rms} = V_m/\sqrt{2} = 12.506/\sqrt{2}=8.84 \text{ V}$$

$$V_{DC} = 2V_m/\pi = 7.961 \text{ V}$$

$$\gamma = \sqrt{(V_{rms}/V_{DC})^2 - 1}$$
$$= 0.482$$

	Vm		Vrms		VDC		γ	
Half-wave Rectifier	Theoretical	Multi sim	Theoretical	Multi sim	Theoretical	Multi sim	Theoretical	Multi sim
	14.14V	13.109V	7.07V	6.55V	4.50V	4.172V	1.211V	1.210V
Full-wave Rectifier	Theoretical	Multi sim	Theoretical	Multi sim	Theoretical	Multi sim	Theoretical	Multi sim
	14.14V	12.506V	10V	8.84V	9.003V	7.961V	0.483V	0.482V