

DATE:18.01.2021

NAME : PRATHAPANI SATWIKI

REG.NO. : 20BCD7160

Experiment no. 2

Date:18.01.2021

Objective : To Verify KCL And KVL Equations

Software used : NI Multisim

Theory :

1)Theory for KCL:

Junction is a point where three or more components of a circuit meet .


Kirchhoff's Current Law states that “ The sum of the currents flowing towards the junction is equal to the sum of the currents flowing away from the junction ” .

In another way we can say that “The algebraic sum of currents at a junction is zero” . **i.e. $\sum I = 0$.**

Let us prove Kirchhoff's current law by taking one circuit .

In the given circuit we have
1kohm,1kohm,0.8kohm resistors connected in

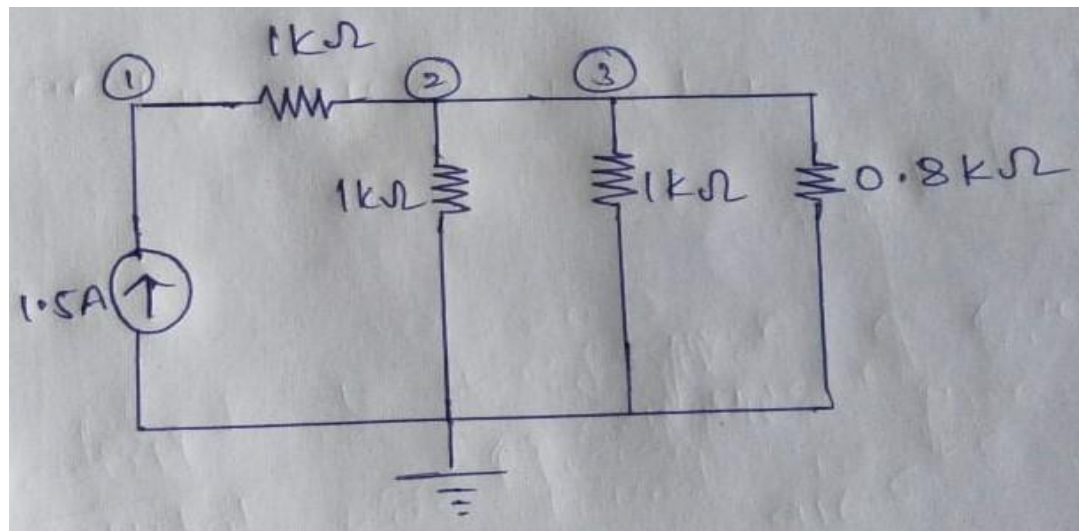parallel and these three resistors connected to 1kohm resistor in series .




Let us assume that the current at node 2 is divided into two currents as i_2, i_3 and current at node 3 is divided into two currents as i_4, i_5 .

According to kirchhoff's law $1.5A = i_2 + i_3$,

$$i_2 = i_4 + i_5$$

Now let's design the circuit in Multisim and see the results .

CIRCUIT DIAGRAM :

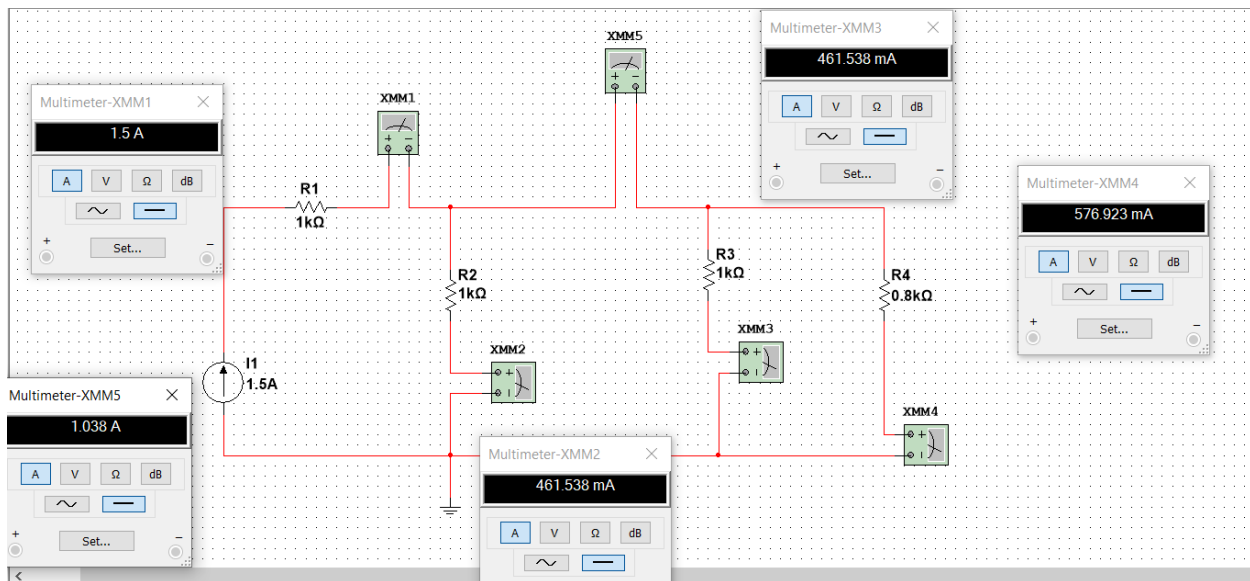

RESULTS AND OBSERVATIONS :

After designing the circuit in Multisim . To find the current by using multimeter across each resistor.

$$i_2 = 1.038 \text{ A}$$

Current across R_2 , i.e. i_3 is 461.538mA

Current across R_3 , i.e. i_4 is 461.538mA

Current across R_4 , i.e. i_5 is 576.923mA

Now according to Kirchhoff's current law :

$$\begin{aligned} 1.5\text{A} &= i_2 + i_3 \\ &= 1.038 + 0.461 \\ &= 1.5\text{A} \end{aligned}$$


Hence by using Multisim Kirchhoff's current law is proved .

2) Theory for KVL :

Kirchhoff's Voltage Law states that "The algebraic sum of all voltages around any closed loop in a circuit is equal to zero". **i.e.** $\sum V = 0$.

In another way we can say that "The sum of all the potential differences around the loop must be equal to zero .

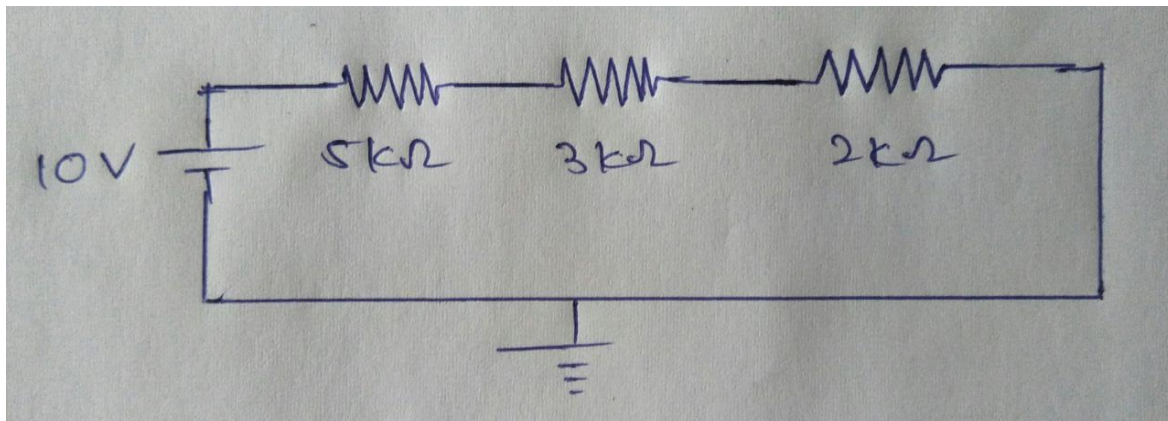Let's take an example to prove kirchhoff's voltage law



Here 5kohm,3kohm,2kohm resistor connected in parallel .

Let us assume that the current flowing through the circuit is I and voltage across 5kohm,3kohm,2kohm is V_1, V_2, V_3 .

According to KVL,

$$10V - V_1 - V_2 - V_3 = 0$$

$$10V = V_1 + V_2 + V_3.$$

As all the resistors connected in series is $I = 10v / (5+3+2)ohm = 1$ milliampere.

As all the resistors are connected in series , the current will remain same .

$$\text{So , } V_1 = 5 * 1 = 5 \text{ Volts}$$

$$V_2 = 3 * 1 = 3 \text{ Volts}$$

$$V_3 = 2 * 1 = 2 \text{ Volts}$$


Now according to Kirchhoff's law ,

$$10V = V_1 + V_2 + V_3$$

$$= 5 + 3 + 2 = 10V \text{ (Kirchhoff's}$$

voltage law is theoretically proved)

CIRCUIT DIAGRAM :

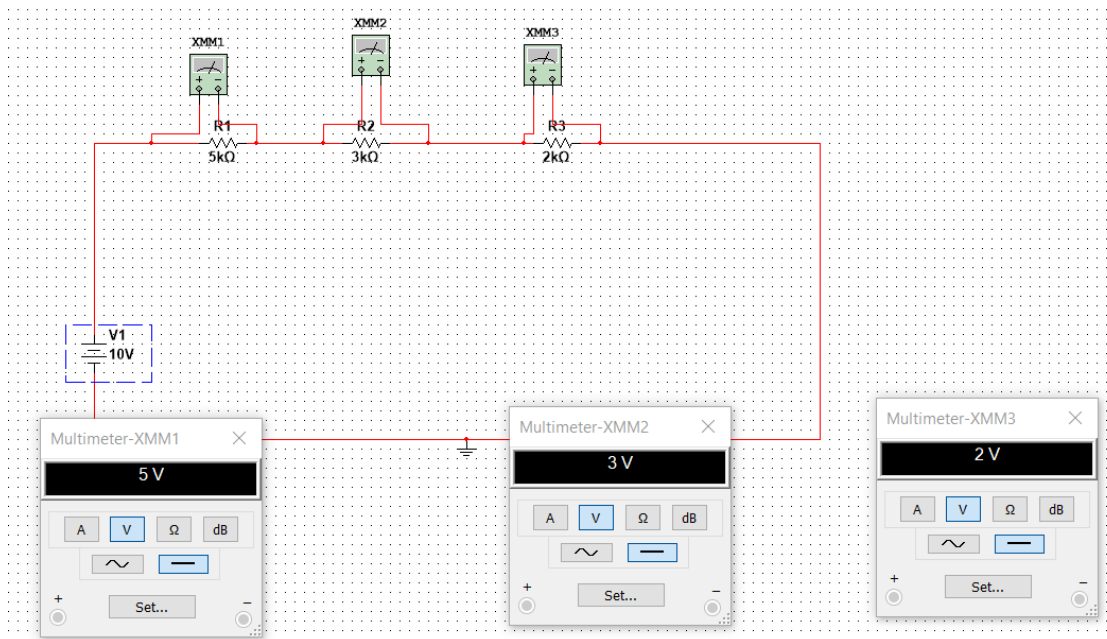

RESULTS AND OBSERVATIONS :

When the circuit was constructed on Multisim the results obtained were same as the results we got while theoretically equating Kirchhoff's voltage equation . As you can see by using multimeter in Multisim the voltage across V1 i.e.5k ohm is 5V , across V2 i.e.3k ohm and across V3 i.e. 2K ohm is 2V . By adding all together we get 10V same as the voltage proved across the circuit 10V .

Hence Kirchhoff's Voltage law is proved .

